

EECT/CE 6325 VLSI Design - Fall 2022  
Department of Electrical & Computer Engineering  
The University of Texas at Dallas



# Non-Overlapping 5 Bit Sequence Detector

## Project 1: Verilog Design

Submitted By

Sai Shantan Nagelli

SXN210083

Sanjay Sankarasubramanian

SXS220137

Surya Ramesh Kumar


SXR220066

## Aim


Our project aims to design a 5 bit non overlapping sequence detector. The circuit takes a stream of bits as input and generates a high output whenever the target sequence is detected. As a non-overlapping sequence detector, the last bit of the detected sequence is not considered as the starting bit of the next sequence.

The sequence detector was designed by developing the State Machines and their corresponding State Tables. From the State Tables, the Boolean expressions for the final circuit are derived using Karnaugh Maps. The sequence detector is realized using three D flipflops and various combinational gates.


## Block Diagram

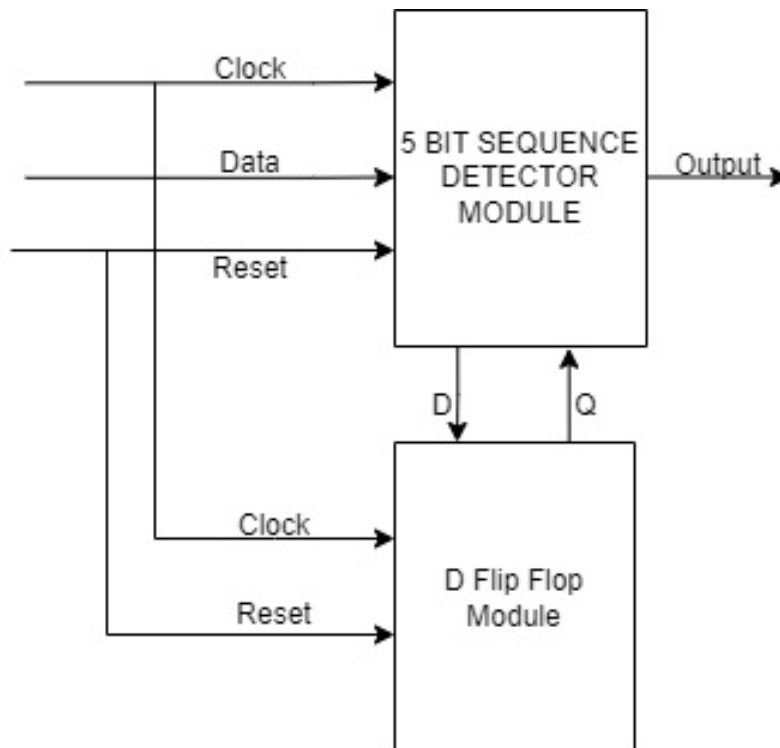


## Test Bench

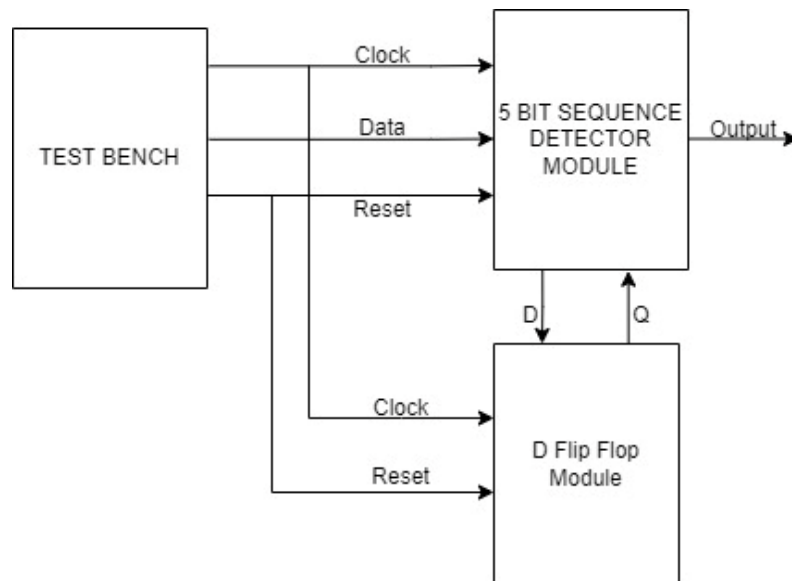

## State Machines

 

State Machine for sequence 10101

 

State Machine for sequence 10101

# State Tables

For Sequence 10101

| State          | Qa | Qb | Qc | X | Next State     | Qa <sub>t+1</sub> | Qb <sub>t+1</sub> | Qc <sub>t+1</sub> | Y |
|----------------|----|----|----|---|----------------|-------------------|-------------------|-------------------|---|
| S <sub>0</sub> | 0  | 0  | 0  | 0 | S <sub>0</sub> | 0                 | 0                 | 0                 | 0 |
| S <sub>0</sub> | 0  | 0  | 0  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>1</sub> | 0  | 0  | 1  | 0 | S <sub>2</sub> | 0                 | 1                 | 0                 | 0 |
| S <sub>1</sub> | 0  | 0  | 1  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>2</sub> | 0  | 1  | 0  | 0 | S <sub>0</sub> | 0                 | 0                 | 0                 | 0 |
| S <sub>2</sub> | 0  | 1  | 0  | 1 | S <sub>3</sub> | 0                 | 1                 | 1                 | 0 |
| S <sub>3</sub> | 0  | 1  | 1  | 0 | S <sub>4</sub> | 1                 | 0                 | 0                 | 0 |
| S <sub>3</sub> | 0  | 1  | 1  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>4</sub> | 1  | 0  | 0  | 0 | S <sub>0</sub> | 0                 | 0                 | 0                 | 0 |
| S <sub>4</sub> | 1  | 0  | 0  | 1 | S <sub>0</sub> | 0                 | 0                 | 0                 | 1 |

For Sequence 10001

| State          | Qa | Qb | Qc | X | Next State     | Qa <sub>t+1</sub> | Qb <sub>t+1</sub> | Qc <sub>t+1</sub> | Y |
|----------------|----|----|----|---|----------------|-------------------|-------------------|-------------------|---|
| S <sub>0</sub> | 0  | 0  | 0  | 0 | S <sub>0</sub> | 0                 | 0                 | 0                 | 0 |
| S <sub>0</sub> | 0  | 0  | 0  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>1</sub> | 0  | 0  | 1  | 0 | S <sub>2</sub> | 0                 | 1                 | 0                 | 0 |
| S <sub>1</sub> | 0  | 0  | 1  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>2</sub> | 0  | 1  | 0  | 0 | S <sub>3</sub> | 0                 | 1                 | 1                 | 0 |
| S <sub>2</sub> | 0  | 1  | 0  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>3</sub> | 0  | 1  | 1  | 0 | S <sub>4</sub> | 1                 | 0                 | 0                 | 0 |
| S <sub>3</sub> | 0  | 1  | 1  | 1 | S <sub>1</sub> | 0                 | 0                 | 1                 | 0 |
| S <sub>4</sub> | 1  | 0  | 0  | 0 | S <sub>0</sub> | 0                 | 0                 | 0                 | 0 |
| S <sub>4</sub> | 1  | 0  | 0  | 1 | S <sub>0</sub> | 0                 | 0                 | 0                 | 1 |

$$Y = Q_a \bar{Q}_b \bar{Q}_c X$$

# Karnaugh Map Simplification

For sequence 10101

D<sub>a</sub>

|                  |                               |   |  |  |
|------------------|-------------------------------|---|--|--|
|                  | Q <sub>a</sub> Q <sub>b</sub> |   |  |  |
| Q <sub>c</sub> X |                               |   |  |  |
|                  |                               |   |  |  |
|                  |                               |   |  |  |
|                  |                               | 1 |  |  |

$$D_a = \overline{Q}_a Q_b Q_c \overline{X}$$

D<sub>b</sub>

|                  |                               |   |  |  |
|------------------|-------------------------------|---|--|--|
|                  | Q <sub>a</sub> Q <sub>b</sub> |   |  |  |
| Q <sub>c</sub> X |                               |   |  |  |
|                  |                               | 1 |  |  |
|                  |                               |   |  |  |
|                  | 1                             |   |  |  |

$$D_b = \overline{Q}_a Q_b \overline{Q}_c X + \overline{Q}_a \overline{Q}_b Q_c \overline{X}$$


D<sub>c</sub>

|                  |                               |   |  |  |
|------------------|-------------------------------|---|--|--|
|                  | Q <sub>a</sub> Q <sub>b</sub> |   |  |  |
| Q <sub>c</sub> X |                               |   |  |  |
|                  | 1                             | 1 |  |  |
|                  | 1                             | 1 |  |  |
|                  |                               |   |  |  |

$$D_c = \overline{Q}_a X$$

# Logic Gate Diagram

For Sequence 10101

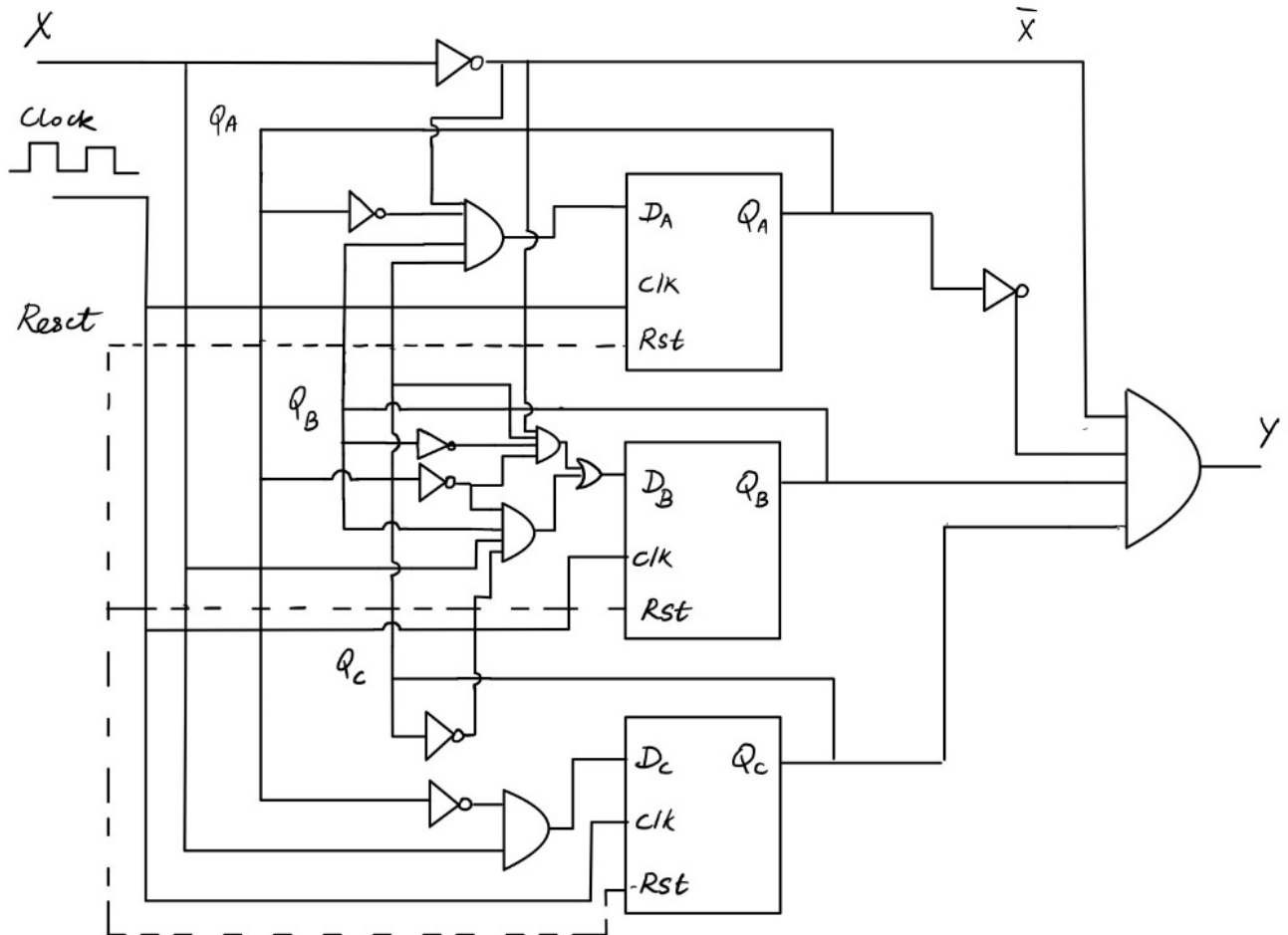

Logic gate diagram for sequence 10101

Our logic gate circuit for the detection of sequence 10101 utilizes three D flipflops ( $D_A$ ,  $D_B$  and  $D_C$ ) and combinational gates AND, OR and Inverters. The same K-Map simplification and Logic gate circuit design seen above has been followed for the '10001' sequence detector as well.

# Verilog Code

```
//EECT/CE 6325 VLSI Design -Fall 2022
//PROJECT - 1: Verilog/VHD

//Members: Sai Shantan Nagelli (sxn210083), Sanjay Sankarasubramanian (sxs220137), Surya Ramesh Kumar (sxr220066)

//5 Bit Non Overlapping Sequence Detector (10101 & 10001)

//D Flip Flop Module

module dff (
    input clock,          // Clock input to drive the flip flop
    input reset,          // Reset input to reset flip flop state
    input d,              // Data input to flip flop
    output reg q          // Output of flip flop - Register Q
);

always @ (posedge clock or posedge reset) //Flip flop works on either positive edge of clock or reset inputs
begin
    if(reset)              //When Reset pin set to 1, output of flipflop 'q' is reset to 0
        q <= 0;
    else
        q <= d;           //On positive edge of clock, output of flipflop 'q' is set to Data input 'd'
    end
endmodule

// Module to detect 5 bit sequence 10101

module seq_det_10101 (
    input clock,          // Clock input to drive the flip flop
    input reset,          // Reset input to reset the flip flop state
    input data,           // Data input to flip flop
    output detected_10101 //Output - 0 when sequence is not detected, 1 when sequence is detected
);

wire [2:0] D1;          //3-bit wire for flipflop data inputs
wire [2:0] Q1;          //3-bit wire for flipflop output

//Boolean Expressions from reducing State Table using K-Map

assign D1[0] = (~Q1[0] & Q1[1] & Q1[2] & ~data); //Input to flipflop A
assign D1[1] = (~Q1[0] & Q1[1] & ~Q1[2] & data) | (~Q1[0] & ~Q1[1] & Q1[2] & ~data); //Input to flipflop B
assign D1[2] = (~Q1[0] & data); //Input to flipflop C
assign detected_10101 = ~Q1[1] & data & Q1[0] & ~Q1[2]; //Sequence detection output for 10101

//Passing input and output parameters to the flipflops (A, B and C)

dff DA (clock, reset, D1[0], Q1[0]);
dff DB (clock, reset, D1[1], Q1[1]);
dff DC (clock, reset, D1[2], Q1[2]);

endmodule

// Module to detect 5 bit sequence 10001

module seq_det_10001 (
    input clock,          // Clock input to drive the flip flop
    input reset,          // Reset input to reset the flip flop state
    input data,           // Data input to flip flop
    output detected_10001 //Output - 0 when sequence is not detected, 1 when sequence is detected
);

wire [2:0] D2;          //3-bit wire for flipflop data inputs
wire [2:0] Q2;          //3-bit wire for flipflop output

//Boolean Expressions from reducing State Table using K-Map

assign D2[0] = (~Q2[0] & Q2[1] & Q2[2] & ~data); //Input to flipflop D
assign D2[1] = (~Q2[0] & Q2[1] & ~Q2[2] & ~data) | (~Q2[0] & ~Q2[1] & Q2[2] & ~data); //Input to flipflop E
assign D2[2] = (~Q2[0] & data) + (~Q2[0] & Q2[1] & ~Q2[2]); //Input to flipflop F
assign detected_10001 = ~Q2[1] & data & Q2[0] & ~Q2[2]; //Sequence detection output for 10001
```

```

//Passing input and output parameters to the flipflops (D, E and F)

dff DD (clock, reset, D2[0], Q2[0]);
dff DE (clock, reset, D2[1], Q2[1]);
dff DF (clock, reset, D2[2], Q2[2]);

endmodule

```

## Testbench Code

```

module seqDetect_tb;

    reg clock;
    reg reset;
    reg data;

    wire detected_10001;
    wire detected_10101;

    //Link main modules with testbench

    seq_det_10001 uut1 (.clock(clock),.reset(reset),.data(data),.detected_10001(detected_10001));
    seq_det_10101 uut2 (.clock(clock),.reset(reset),.data(data),.detected_10101(detected_10101));

    initial begin

        //Initialize Inputs

        clock = 1'b0;
        reset = 1'b1;
        data = 0;

        #5 reset = 1'b0;    //Unset reset pin

        //Input sequence stream

        #10 data = 0;
        #10 data = 1;
        #10 data = 0;
        #10 data = 1;
        #10 data = 0;
        #10 data = 1;    //Overlap = Not counted as first bit of sequence 10101
        #10 data = 0;
        #10 data = 1;
        #10 data = 0;
        #10 data = 1;
        #10 data = 1;
        #10 data = 1;
        #10 data = 0;
        #10 data = 0;
        #10 data = 0;
        #10 data = 1;    //Overlap = Not counted as first bit of sequence 10001
        #10 data = 0;
        #10 data = 0;
        #10 data = 0;
        #10 data = 1;
    end


    initial #250 $finish;    //Finish simulation
    always #5 clock = ~clock;    //Switch clock from 0 to 1 for every 5 nanoseconds

endmodule

```



## Output Wave Form

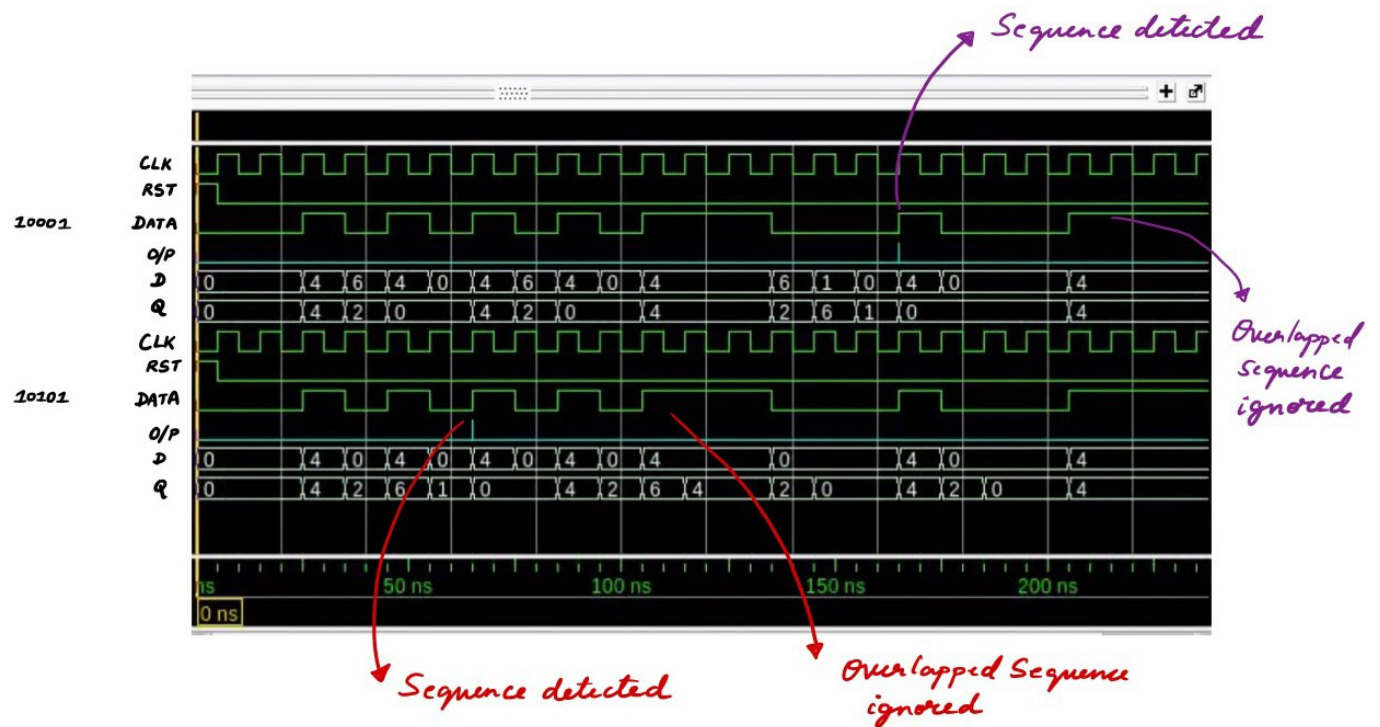

## Results

From the output waveform, it is observed that the output goes high only when the 5-bit sequences '10101' or '10001' are detected. Based on our testbench input, we receive the sequences '10101' and '10001' at times 65 and 175 nanoseconds respectively. During these times, we get a high output which corresponds to the peaks observed in the graph (Cyan O/P). During these times, we also have continuing overlapping sequences, and these are not detected.